

Example: 9.6

$i_1(t) = 4 \cos(\omega t + 30^\circ)$, $i_2(t) = 5 \sin(\omega t - 20^\circ)$. Find the sum.

Solution:

$$i_1(t) = 4 \cos(\omega t + 30^\circ) \\ = 4 \angle 30^\circ i$$

$$i_2(t) = 5 \sin(\omega t - 20^\circ) \\ = 5 \cos(\omega t - 20^\circ - 90^\circ) \\ = 5 \cos(\omega t - 110^\circ) \\ = 5 \angle -110^\circ i$$

Now, the sum is,

$$i_1(t) + i_2(t) \\ = (4 \angle 30^\circ) + (5 \angle -110^\circ) \\ = 3.2184 \angle -56.9^\circ.$$

Note: Using calculator

CMPLX MODE

$$\begin{aligned} & \text{4} \xrightarrow{\text{SHIFT}} \text{30} \xrightarrow{+} \text{5} \xrightarrow{\text{SHIFT}} \text{-110} \\ & \text{4} \xrightarrow{\text{SHIFT}} \text{30} \xrightarrow{+} \text{5} \xrightarrow{\text{SHIFT}} \text{-110} \\ & \text{= 3.2184} \xrightarrow{\text{SHIFT}} \text{-56.9} \end{aligned}$$

Practice problem: 9.6

$$v_1 = -10 \sin(\omega t - 30^\circ)$$

$$v_2 = 20 \cos(\omega t + 45^\circ) \text{ find the sum.}$$

Solution:

$$\begin{aligned} v_1 &= -10 \sin(\omega t - 30^\circ) \\ &= 10 \cos(\omega t - 30^\circ + 90^\circ) \\ &= 10 \cos(\omega t + 60^\circ) \\ &= 10 \angle 60^\circ \end{aligned}$$

$$\begin{aligned} v_2 &= 20 \cos(\omega t + 45^\circ) \\ &= 20 \angle 45^\circ \end{aligned}$$


using calculator
 $(10 \angle 60^\circ) + (20 \angle 45^\circ) =$

Now, the sum is,

$$\begin{aligned} v_1 + v_2 &= (10 \angle 60^\circ) + (20 \angle 45^\circ) \\ &= 19.14 \angle 22.80^\circ \end{aligned}$$

Example: 9.9

$$v_s = 10 \cos(4t + 0^\circ)$$

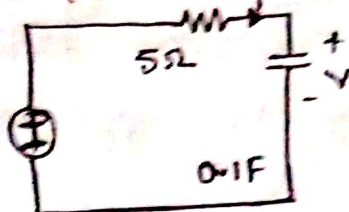

find $i(t)$ and $v(t)$.

Note:

$$C \frac{1}{T} \rightarrow X_C = \frac{1}{j2\pi fC} = \frac{1}{j\omega C}$$

$$L \rightarrow X_L = j2\pi fL = j\omega L$$

Solution:

$$V_s = 10 \cos(4t + 0^\circ)$$

$$= 10 \angle 0^\circ$$

$$\therefore i(t) = \frac{V}{Z}$$

$$= \frac{10 \angle 0^\circ}{5 - j2.5}$$

$$= 1.788 \angle 26.56^\circ \text{ A}$$


$$\therefore v(t) = I X_c$$

$$= (1.788 \angle 26.56^\circ) \times (-j2.5)$$

$$= 4.47 \angle -116.63^\circ \text{ V}$$

Practice problem: 9.9
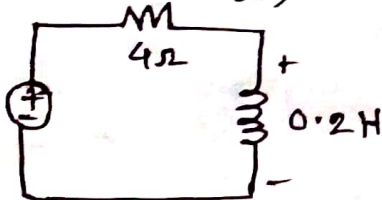
$$V_s = 20 \sin(10t + 30^\circ) \text{ V}$$



find the $i(t)$ and $v(t)$.

Solution:

$$V_s = 20 \sin(10t + 30^\circ)$$

$$= 20 \cos(10t + 30^\circ - 90^\circ)$$

$$= 20 \cos(10t - 60^\circ)$$

$$= 20 \cos(10t - 60^\circ)$$

$$= 20 \angle -60^\circ$$

$$A_c = I = \frac{V}{Z}$$

$$\therefore X_c = \frac{1}{j2\pi fC}$$


$$= \frac{1}{j\omega C}$$

$$= \frac{1}{j4 \times 0.1} = -j2.5 \Omega$$

$$= -j2.5 \Omega$$

$$\therefore Z = 5 - j2.5 \Omega$$

Note: Using calculator

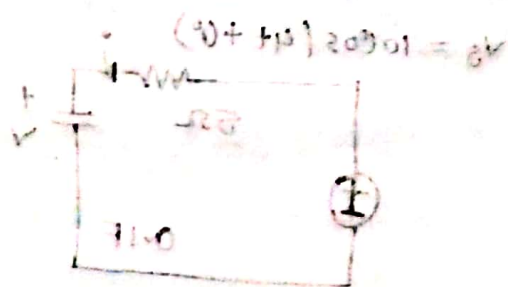

$$i(t) = \frac{v}{Z} = \frac{20 \angle -67^\circ}{4 + j2}$$

$$= 4.47 \angle -86.66^\circ$$

$$X_L = j\omega L$$

$$= 50 \times 0.2$$

$$= 10j$$

$$Z = R + jX_L$$

$$= 4 + j10$$

$$\therefore v(t) = I Z$$

$$= (4.47 \angle -86.66^\circ) \times 2j$$

$$= 8.94 \angle 3.44^\circ$$

chapter 11

AC power Analysis

Example 11.1

Given that $v(t) = 120 \cos(322t + 45^\circ)$ V and $i(t) = 10 \cos(322t - 15^\circ)$ A find the instantaneous power and the average power absorbed by the passive linear network.

Solution:

$$v(t) = 120 \cos(322t + 45^\circ) \text{ V}$$

$$i(t) = 10 \cos(322t - 15^\circ) \text{ A}$$

$$V_m = 120$$

$$I_m = 10$$

$$\begin{aligned}
 P(t) &= \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) + \frac{V_m I_m}{2} \cos(2\omega t + \theta_v + \theta_i) \\
 &= \frac{120 \times 10}{2} \cos(45^\circ + 10^\circ) + \frac{120 \times 10}{2} \cos(2 \times 322t + 45^\circ + 10^\circ) \\
 &= 600 \cos 55^\circ + 600 \cos(254t + 35^\circ) \\
 &= 344.14 + 600 \cos(254t + 35^\circ)
 \end{aligned}$$

practice problem: 11.1

$$v(t) = 330 \cos(10t + 20^\circ) \text{ V}$$

$$i(t) = 33 \sin(10t + 60^\circ) \text{ A}$$

find $P(t)$.

Solution:

$$v(t) = 330 \cos(10t + 20^\circ) \text{ V}$$

$$i(t) = 33 \sin(10t + 60^\circ) \text{ A}$$

$$= 33 \cos(10t - 30^\circ) \text{ A}$$

$$V_m = 330$$

$$I_m = 33$$

$$\theta_v = 20^\circ$$

$$\theta_i = 30^\circ \text{ (reference)}$$

$$\begin{aligned}
 P(t) &= \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) + \frac{V_m I_m}{2} \cos(2\omega t + \theta_v + \theta_i) \\
 &= \frac{330 \times 33}{2} \cos(20^\circ + 30^\circ) + \frac{330 \times 33}{2} \cos(2 \times 10t + 20^\circ + 30^\circ) \\
 &= 5445 \cos 50^\circ + 5445 \cos(20t + 50^\circ)
 \end{aligned}$$

Q. Find i_1, i_2, i_3 in the circuit fig 1.1(a).



Fig 1.1

Solution:

loop 1,

$$30i_1 + 10i_1 - 10i_2 + 120 = 0$$

$$\Rightarrow 40i_1 - 10i_2 = -120 \quad \text{--- (1)}$$

loop 2,

$$30i_2 + 10i_2 - 10i_1 + 10i_3 - 10i_1 = 0$$

$$\Rightarrow 10i_1 + 50i_2 - 10i_3 = 0 \quad \text{--- (2)}$$

loop 3,

$$20i_3 + 10i_3 - 10i_2 + 120 = 0$$

$$\Rightarrow 40i_3 - 10i_2 = 120 \quad \text{--- (3)}$$


Using calculator to solve, i_1, i_2, i_3

$$i_1 = -2A$$


$$i_2 = 0$$

$$i_3 = 2A$$

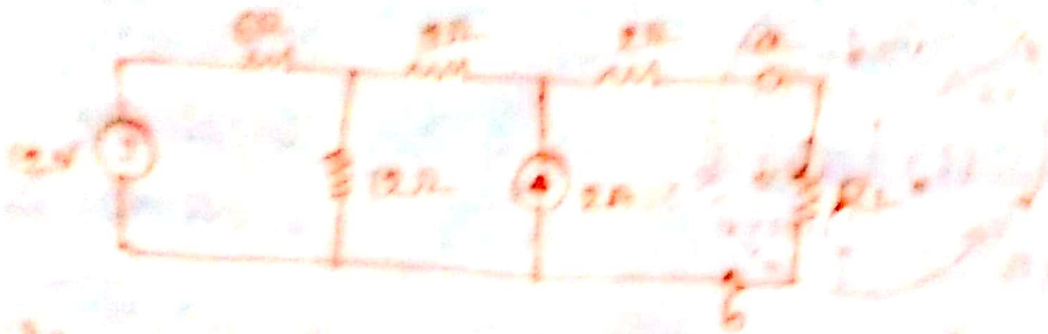Q3. Find the value of R_L for maximum power transfer in the circuit as shown.




Solution:

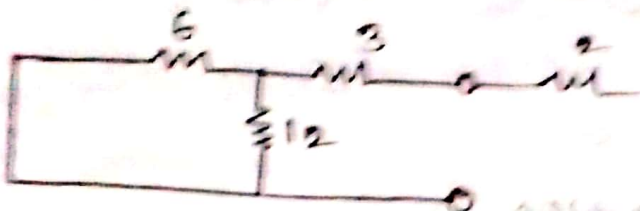

$$R_{th} = (6 \parallel 12) + 3 + 2$$

$$= 9\Omega$$

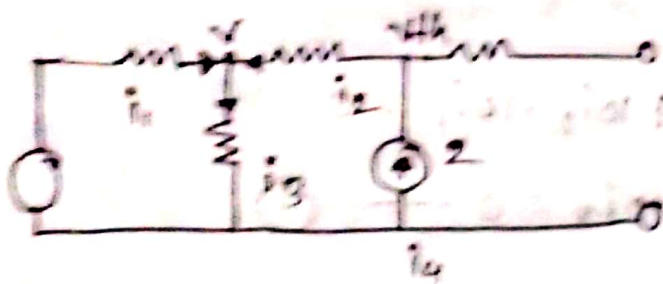

Applying KCL node 1

$$V_{th} \Rightarrow i_1 + i_2 = i_3$$

$$\frac{12-V}{6} + \frac{V_{th}-V}{3} = \frac{V-0}{12}$$

$$\Rightarrow \frac{12-V + 2V_{th} - 2V}{6} = \frac{V}{12}$$

$$\Rightarrow 24 - 6V + 4V_{th} = V$$

$$\Rightarrow 4V_{th} - 2V = -24 \quad \text{--- (1)}$$

node 2

$$i_4 = i_2$$

$$2 = \frac{V_{th} - V}{3}$$


$$\Rightarrow V_{th} - V = 6 \quad \text{--- (1)}$$

① and ② solving we get :

$$V_{th} = 22 \text{ V}$$

$$V = 16 \text{ V}$$

equivalent circuit :

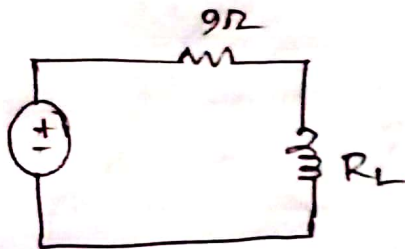

for maximum power $R_L = 9\Omega$ Ans.

and

$$P_{max} = \frac{V_{th}^2}{4 R_{th}}$$

$$= \frac{(22)^2}{4 \times 9}$$

$$= 13.44 \text{ watt} \quad \underline{\text{Ans.}}$$

Theory:

* KCL

* KVL

* Nodal Analysis


* Mesh Analysis

* Thevenin Theorem

* Sine wave * Time period.

* phasor

: divide by $\sqrt{2}$

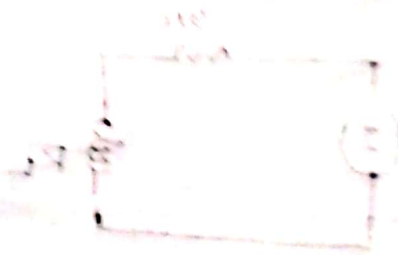

100V

$$\frac{100}{\sqrt{2}} = 70.71 \text{ V}$$
$$\frac{100}{\sqrt{2}} = 70.71 \text{ V}$$
$$\frac{100}{\sqrt{2}} = 70.71 \text{ V}$$

100V

Practice problem: 9.2

Find the phase angle between, $i_1 = -4 \sin(377t + 55^\circ)$ and $i_2 = 5 \cos(377t - 65^\circ)$. Does i_1 lead or lag i_2 ?

Solution:

$$i_1 = -4 \sin(377t + 55^\circ)$$

$$= 4 \cos(377t + 55^\circ + 90^\circ)$$

$$= 4 \cos(377t + 145^\circ)$$

$$= 4 \angle 145^\circ$$

$$i_2 = 5 \cos(377t - 65^\circ)$$

$$= 5 \angle -65^\circ$$

$$\therefore \text{phase angle} = 145^\circ - (-65^\circ)$$


$$= 210^\circ$$

OR, $(145^\circ + 360^\circ) - (-65^\circ)$

$$\therefore \text{phase angle} = 360^\circ - 210^\circ$$

$$= 150^\circ$$

$\therefore i_1$ leads i_2 by 210° .

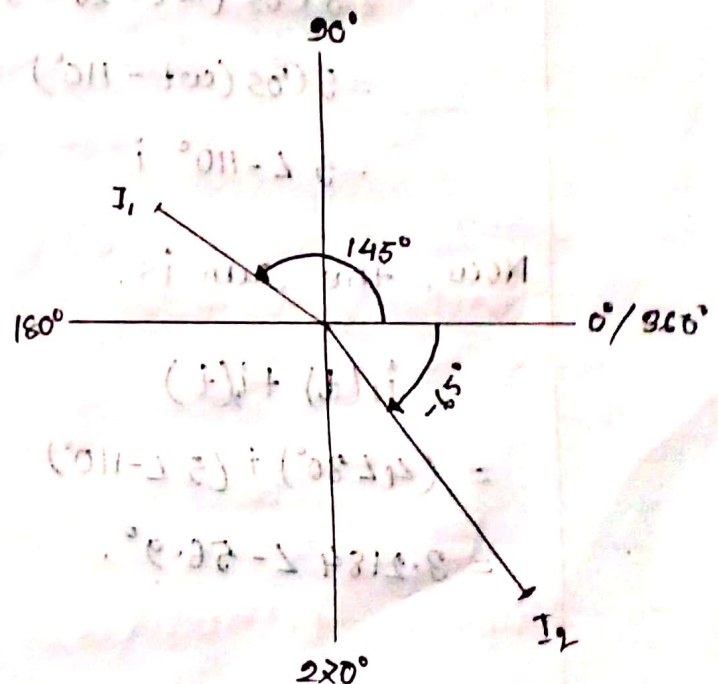

Example 1.8

Calculate the phase angle between $v_1 = 10 \cos(\omega t + 45^\circ)$ and $v_2 = 12 \sin(\omega t - 16^\circ)$, state which quantity is leading.

Solution

$$\begin{aligned} v_1 &= 10 \cos(\omega t + 45^\circ) \\ &= 10 \cos(\omega t + 45^\circ + 180^\circ) \\ &= 10 \cos(\omega t + 225^\circ) \\ &= 10 \angle 225^\circ \end{aligned}$$

$$v_2 = 12 \sin(\omega t - 16^\circ)$$


$$\begin{aligned} \text{shifting up} &= 12 \cos(\omega t - 16^\circ - 90^\circ) \\ &= 12 \cos(\omega t - 106^\circ) \\ &= 12 \cos(\omega t - 106^\circ) \\ &= 12 \angle -106^\circ \end{aligned}$$

$$\therefore \text{phase angle} = 225^\circ - (-106^\circ) = 331^\circ$$

OR

$$\therefore \text{phase angle} = 360^\circ - 29^\circ = 331^\circ$$


$\therefore v_2$ leads v_1 by 29°

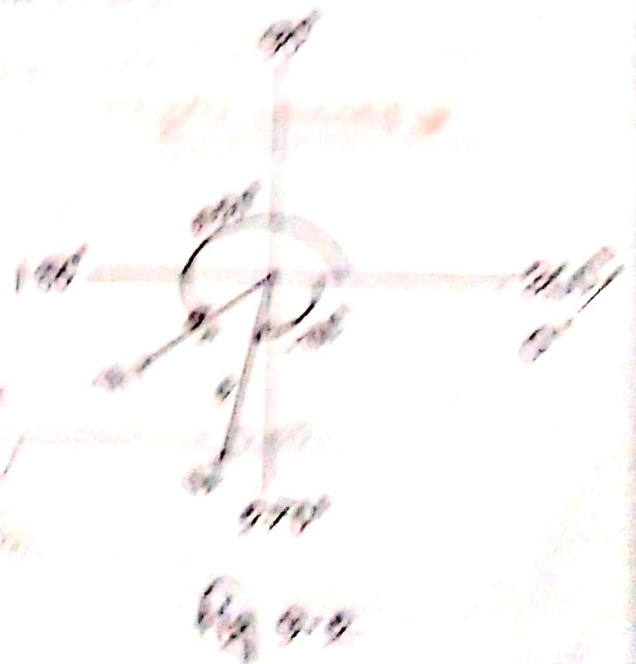

Chapter: 9

Sinusoids and phasors

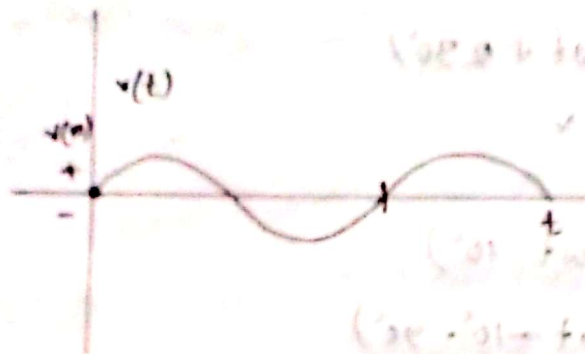Sinusoids: Sinusoids is a signal that has the form of the sine or cosine function.



V_m = magnitude

$$v(t) = V_m \sin \omega t$$

$$v(t) = V_m \cos(\omega t + \theta)$$


phasor angle:

Sinusoidal form:

$$v = V_m \cos \omega t + \theta$$


phasor form:

$$V_m \angle \theta$$

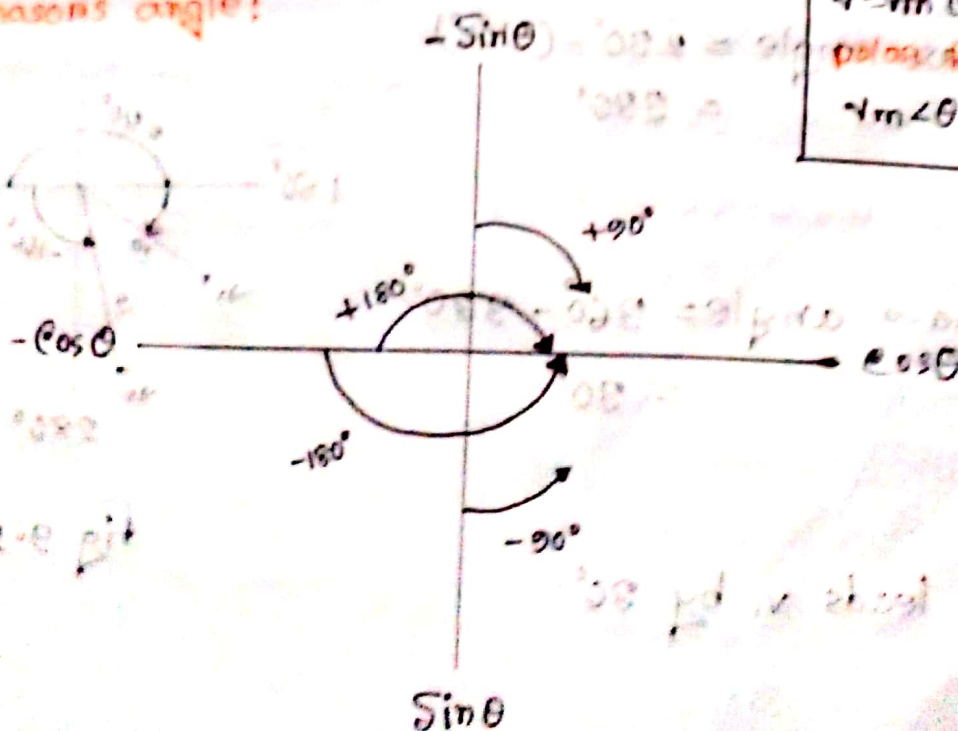

* KCL: The KCL (KIRCHHOFF'S CURRENT LAW) states that in a closed circuit, the entering current at node is equal to the current leaving at the node.


Example:

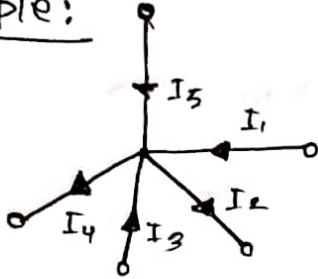

$$\therefore I_1 + I_3 + I_5 = I_2 + I_4$$

* KVL: The KVL (KIRCHHOFF'S VOLTAGE LAW) states that algebraic sum of the voltage at node in a closed circuit is equal to zero.

Example:

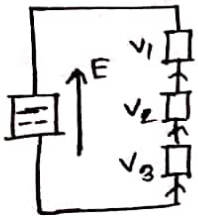


$$\therefore E - V_1 - V_2 - V_3 = 0$$

* phasors: A phasor is a complex number that represents the amplitude and phase a sinusoid.

* Time period: In Ac current, the "time period" is the time it takes for the current to complete one full cycle of its back-and-forth movement.

* KCL: The KCL (KIRCHHOFF'S CURRENT LAW) states that in a closed circuit, the entering current at node is equal to the current leaving at the node.


Example:

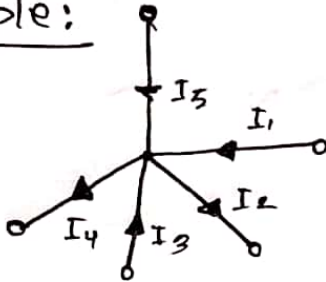

$$\therefore I_1 + I_3 + I_5 = I_2 + I_4$$

* KVL: The KVL (KIRCHHOFF'S VOLTAGE LAW) states that algebraic sum of the voltage at node in a closed circuit is equal to zero.

Example:

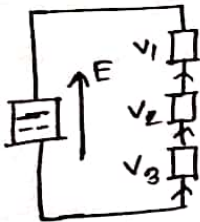

$$\therefore E - V_1 - V_2 - V_3 = 0$$

$$V_R = IR$$

$$= (50.5964 \angle 26.56) \times 3$$

$$= 151.789 \angle 26.56$$

\therefore Average power absorbed by the Resistor,

$$P_{avg} = \frac{1}{2} V_R I_m \cos(\theta_V - \theta_I)$$

$$= \frac{1}{2} \times 151.789 \times 50.5964 \times \cos(26.56 - 26.56)$$

$$= \frac{1}{2} \times 151.789 \times 50.5964 \times \cos(26.56 - 26.56)$$

$$= 3839.98 \text{ watt}$$

\therefore Inductor absorb zero Average power.


\therefore Average power supply by the source,

$$\therefore P_{avg} = \frac{1}{2} V_m I_m \cos(\theta_V - \theta_I)$$

$$= \frac{1}{2} \times 160 \times 50.5964 \times \cos(45 - 26.56)$$

$$= 3839.88 \text{ watt}$$

$$= 3.839 \text{ kW}$$

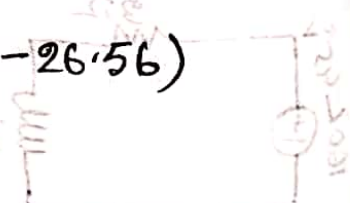

Average power absorbed by the Resistor, $I = 1.18 \text{ A}$

$$P_{avg} = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

$$= \frac{1}{2} \times 4.472 \times 1.18 \times \cos(56.56 - 56.56)$$

$$= 2.49 \text{ Watt}$$

Average power supplied by the source,

$$P_{avg} = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

$$= \frac{1}{2} \times 5 \times 1.18 \times \cos(30^\circ - 56.56^\circ)$$

$$= 2.5 \text{ Watt.}$$

Practic problem; 11.3

In the circuit calculate the average power absorbed by resistor and inductor. find the average power supplied the voltage source.



Solution:

from circuit, $Z = 3 + j1$

$$I = \frac{V}{Z}$$

$$= \frac{160 \angle 45^\circ}{3 + j1}$$

$$= 50.5964 \angle 26.56^\circ$$

We know,


Average power,

$$\begin{aligned} P &= \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) \\ &= \frac{1}{2} \times 800 \times 20 \cos(10^\circ - 30^\circ) \\ &= 7.4174 \text{ kW} \end{aligned}$$

Example: 11.3

for the circuit shown in fig 11.3 find the average power supplied by the source and the average power absorbed by the resistor.

Solution:

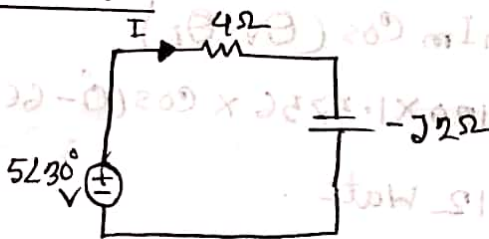

from circuit, $Z = 4 - j2\Omega$

$$I = \frac{V}{Z}$$

$$\Rightarrow \frac{5\angle 30^\circ}{4 - j2\Omega}$$

$$\Rightarrow 1.18\angle 56.56^\circ$$

$$V_R = IR$$

$$= (1.18\angle 56.56^\circ) \times 4$$

$$= 4.72\angle 56.56^\circ$$

Example: 11.2

Calculate the average absorbed by an impedance $Z = 30 - j20\Omega$ when a voltage $V = 120\angle 0^\circ$ is applied across it.

Solution:

$$V = 120\angle 0^\circ$$

$$Z = 30 - j20\Omega$$

Now,

$$I = \frac{V}{Z} = \frac{120\angle 0^\circ}{30 - j20} \\ = 1.56756\angle 66.80^\circ$$

We know,

$$\text{Average power, } P = \frac{1}{2} V_m I_m \cos(\theta_V - \theta_I) \\ = \frac{1}{2} \times 120 \times 1.56756 \times \cos(0^\circ - 66.88^\circ) \\ = 37.12 \text{ Watt}$$

Practice problem: 11.2

A current $I = 20\angle 30^\circ$ A flows through an impedance $Z = 40\angle -22^\circ\Omega$. Find the average power delivered to the impedance.

Solution:

$$I = 20\angle 30^\circ$$

$$Z = 40\angle -22^\circ\Omega$$

Now,

$$V = IZ \\ = (20\angle 30^\circ) \times (40\angle -22^\circ) \\ = \cancel{800\angle 10} \\ = 800\angle 8^\circ$$